

Programming

Section 1: Logic



Abstraction

[https://en.wikipedia.org/wiki/Abstraction_\(computer_science\)](https://en.wikipedia.org/wiki/Abstraction_(computer_science)):

In [software engineering](#) and [computer science](#), **abstraction** is the process of [generalizing concrete](#) details,^[1] such as [attributes](#), away from the study of [objects](#) and [systems](#) to focus attention on details of greater importance.^[2] [Abstraction](#) is a fundamental concept in computer science and [software engineering](#), especially within the [object-oriented programming](#) paradigm.^[3] Examples of this include:


- the usage of [abstract data types](#) to separate usage from working representations of [data](#) within [programs](#);^[4]
- the concept of [functions](#) or subroutines which represent a specific way of implementing [control flow](#);
- the process of reorganizing common behavior from groups of non-abstract [classes](#) into abstract classes using [inheritance](#) and [sub-classes](#), as seen in [object-oriented programming](#) languages.

Transistors

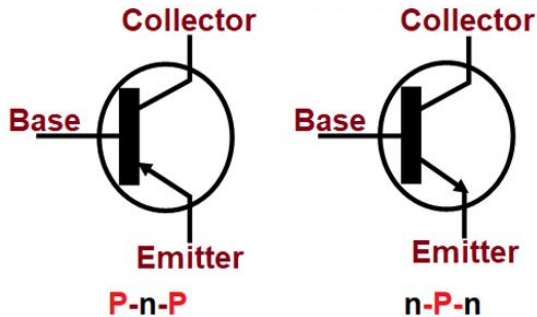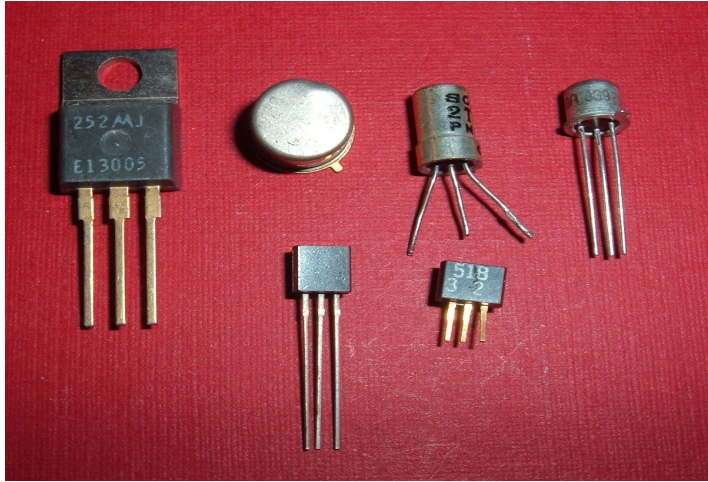


- Basic building block of modern electronics
- Can be thought of as a switch
- The Base controls the “on” and “off” between the Collector and Emitter


PNP switching output

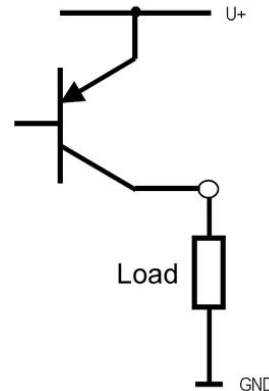

NPN switching output

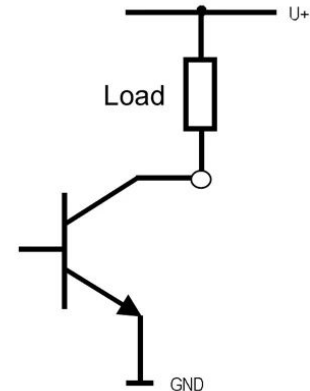


Transistor used as a “switch”

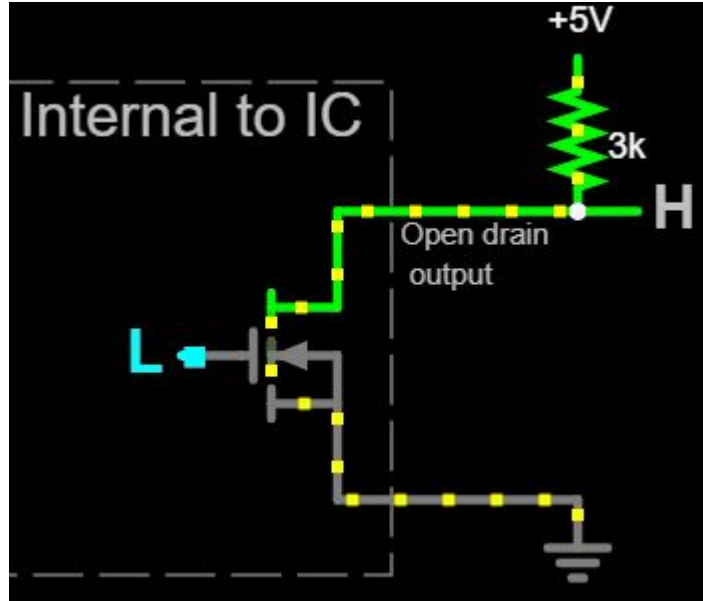


- Switching “on” provides a ground in this scenario. It can be the other way around.
- Using the transistor as a switch allows us to combine multiples to create logic

Not Gate

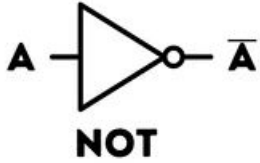

NOT Gate	
A	\overline{A}
0	1
1	0

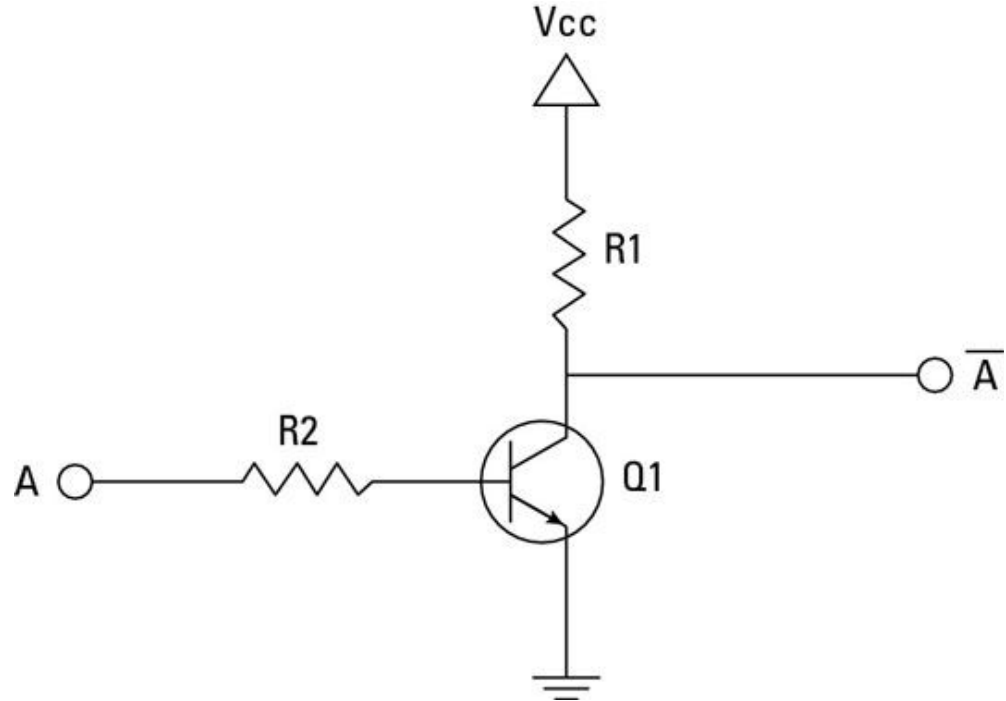


And Gate

2 - input AND gate



A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

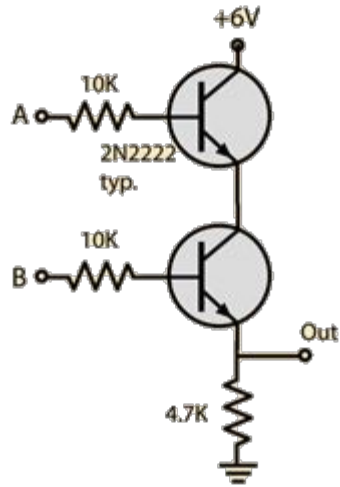


NAND Gate


$$X = \overline{A \cdot B}$$



A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

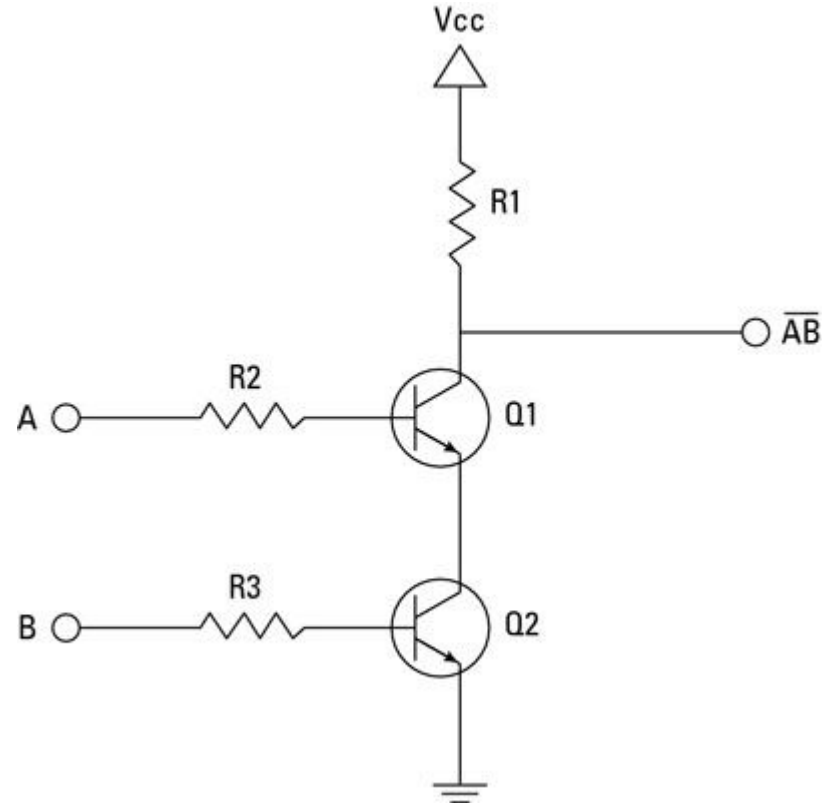


OR Gate

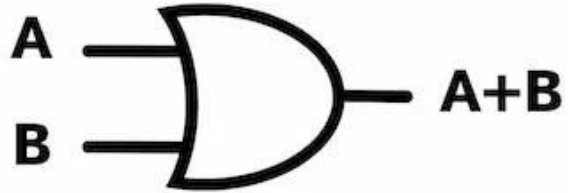


2 input OR gate


A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

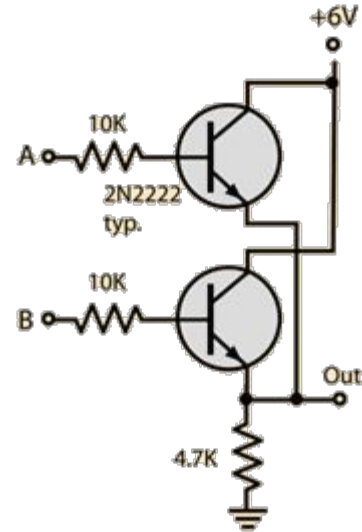


NOR Gate

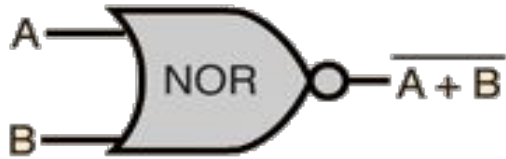


A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

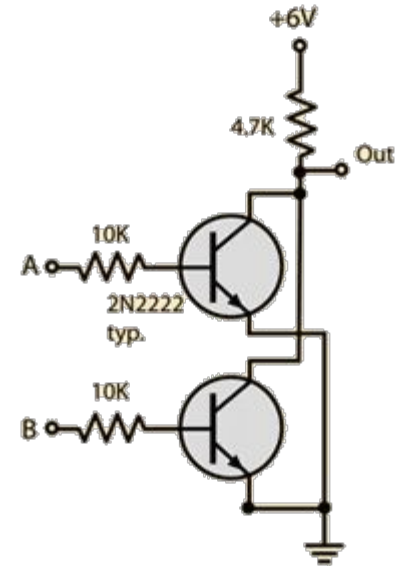

XOR Gate

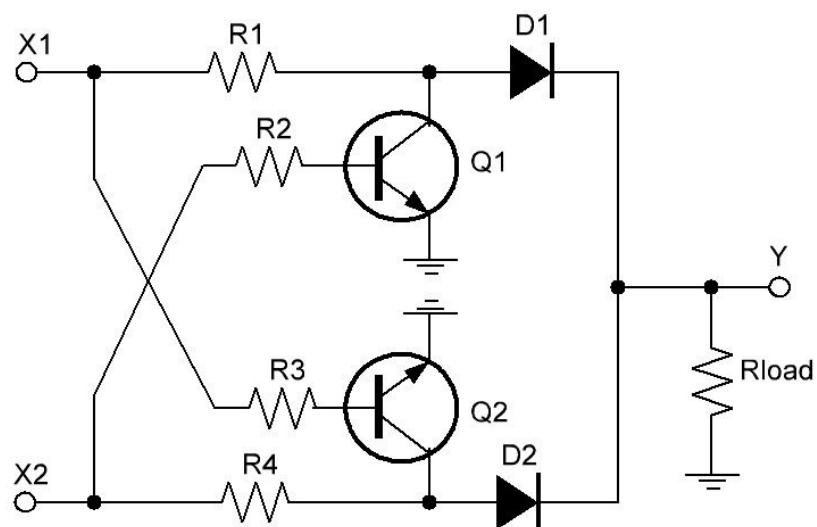


$$X = A \oplus B$$

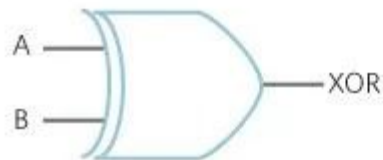


A	B	XOR
0	0	0
0	1	1
1	0	1
1	1	0

SR (Set-Reset) Latch


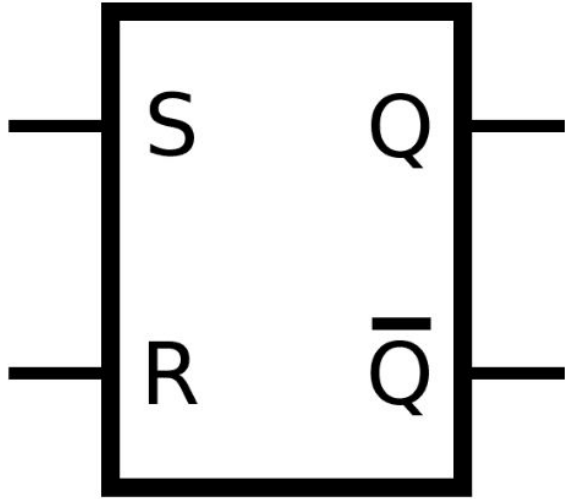


S	R	Q	\bar{Q}
0	0	1	0
0	0	0	1
0	1	0	1
1	0	1	0
1	1	0	0



SR Latch

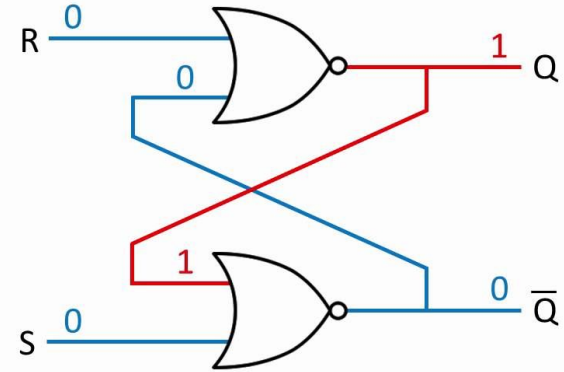

D Latch

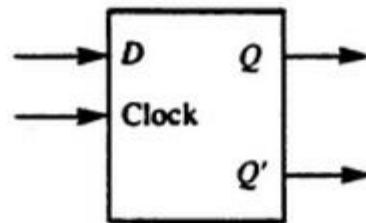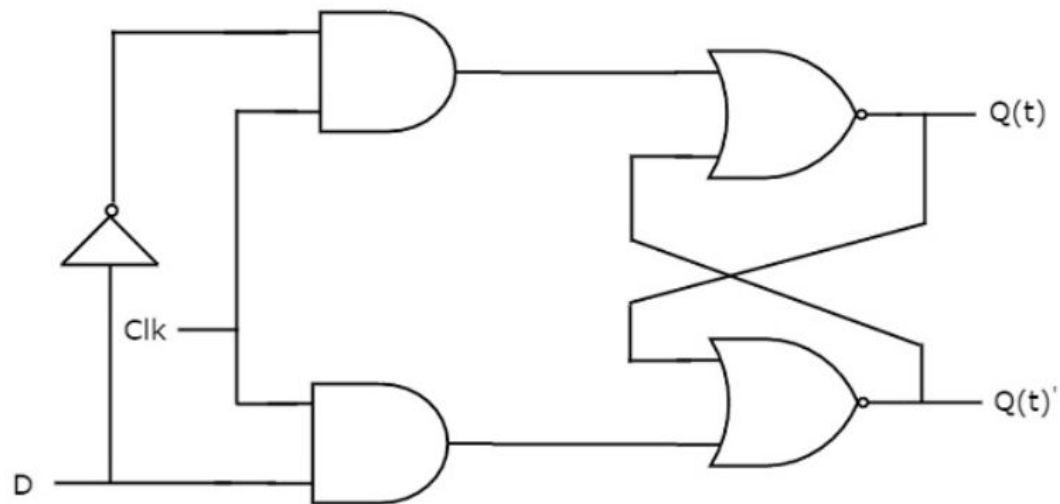



JK Flip Flop

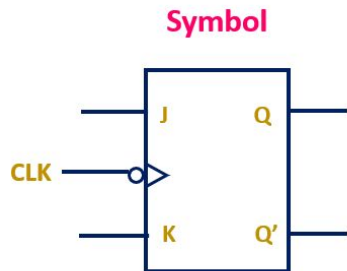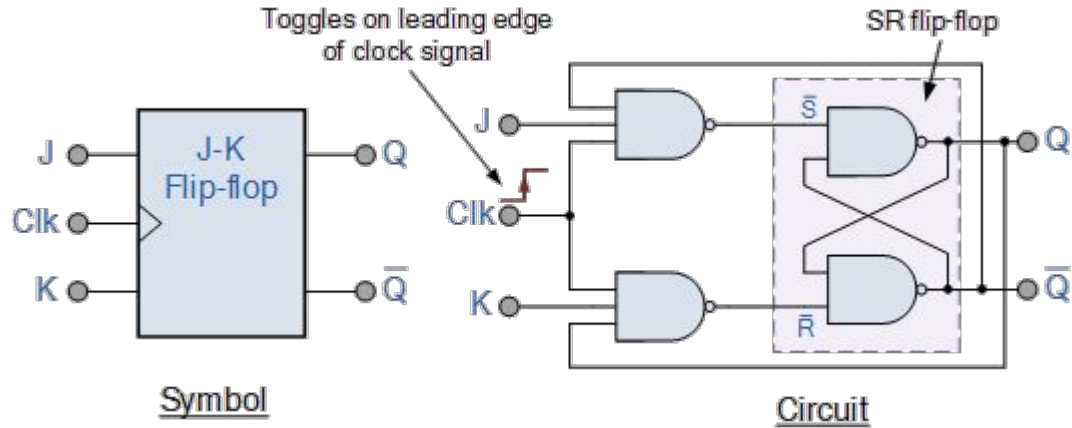




Truth Table

CLK	J	K	Q_{n+1}
↓	0	0	Q_n
↓	0	1	0
↓	1	0	1
↓	1	1	Q_n'


1 Bit full adder

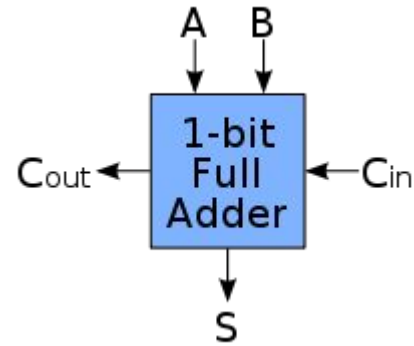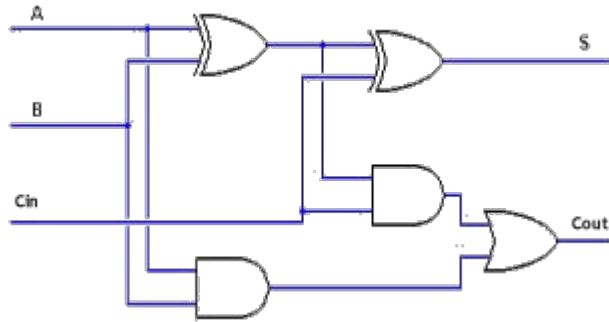







Multiplexer

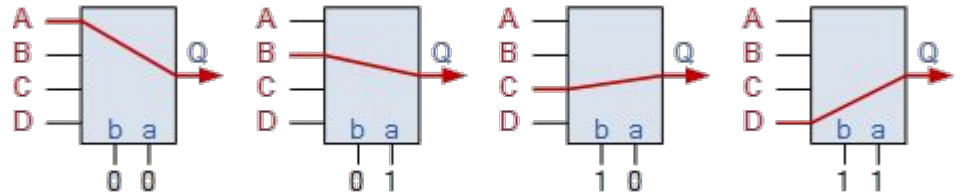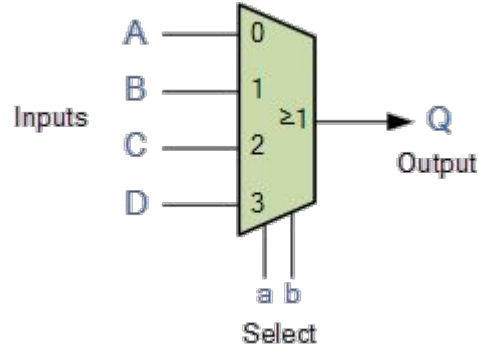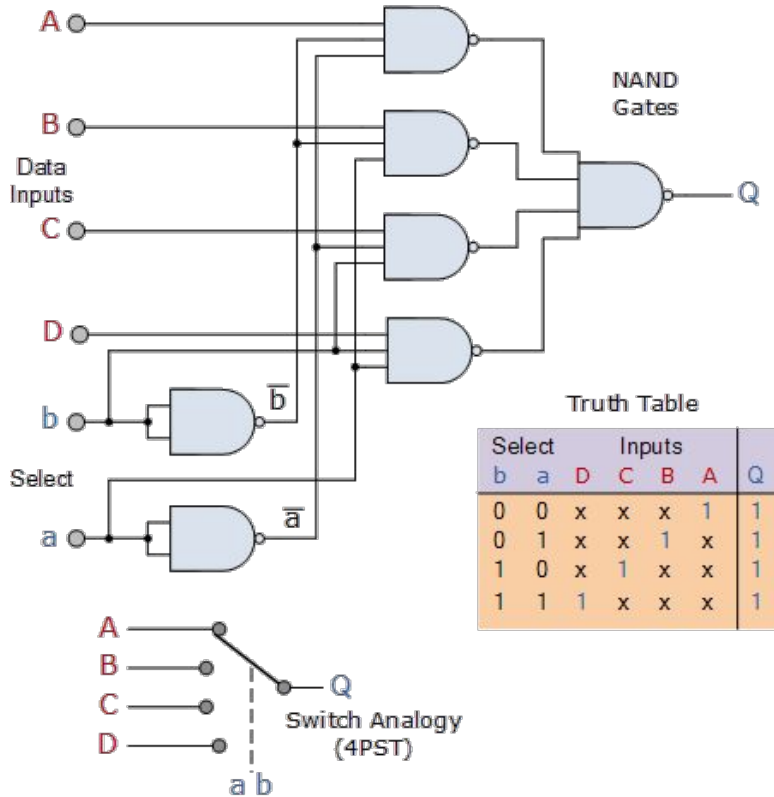

Multiplexer in data bus

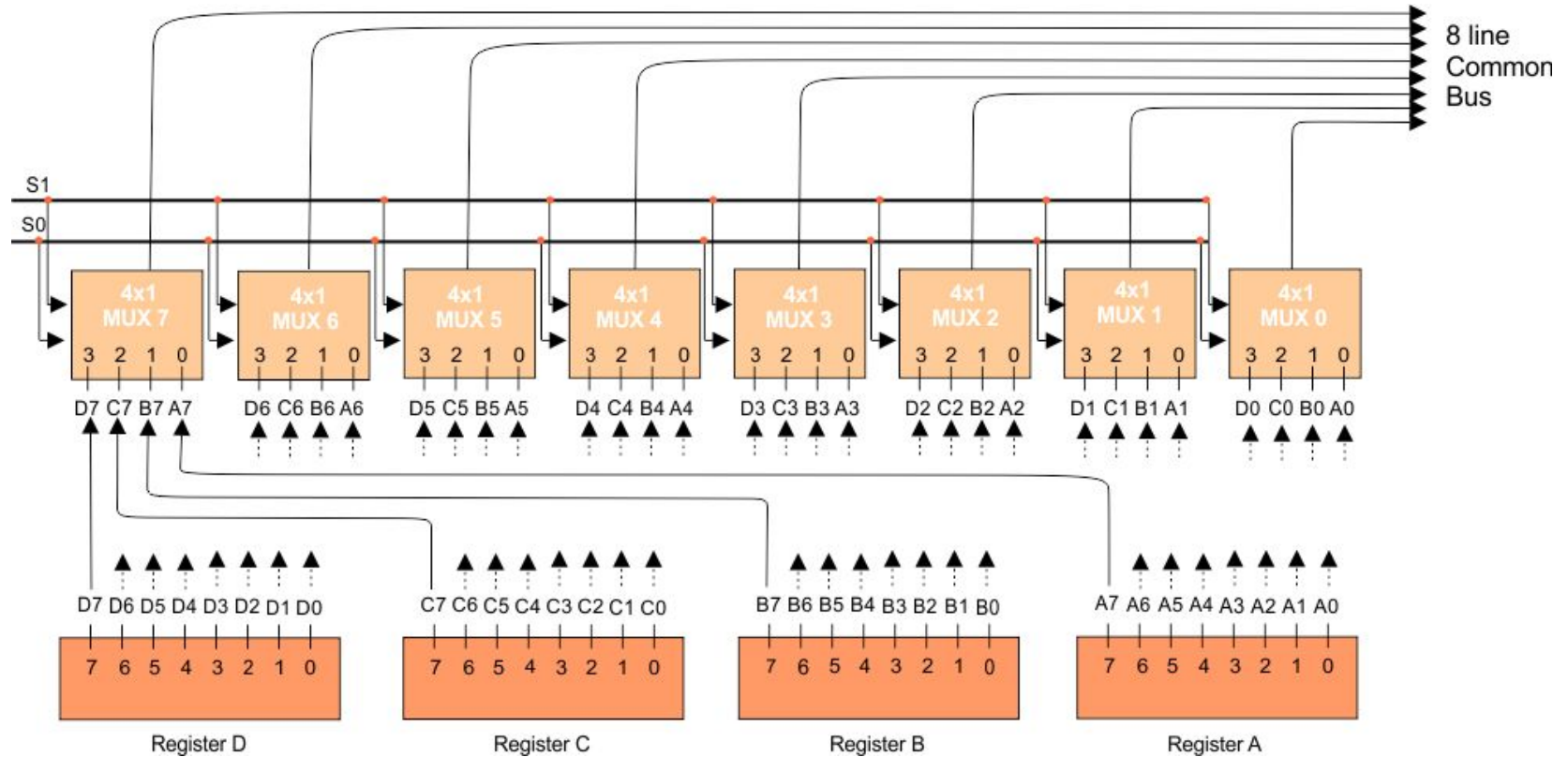

Demultiplexer

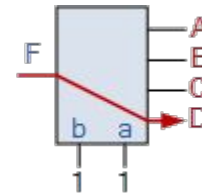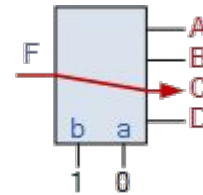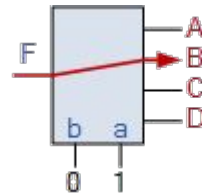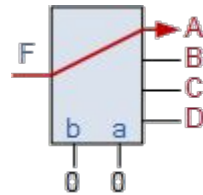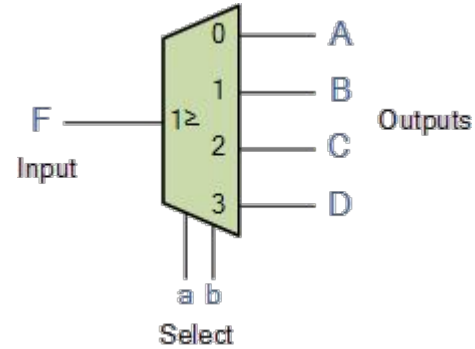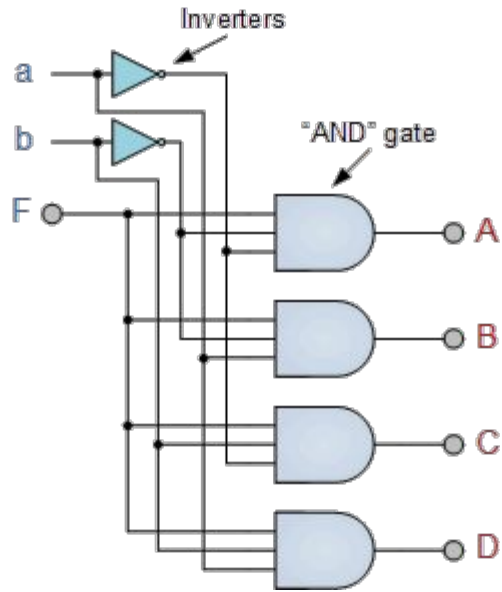

7400 Series Integrated Circuits


A lot of logic chips are still available today:

https://en.wikipedia.org/wiki/List_of_7400-series_integrated_circuits


Overview

- Transistors are combined and abstracted into logic symbols
- Logic symbols are combined and abstracted into latch symbols, De/Multiplexers
- All of that is combined to create RAM, memory busses, etc.


ALU

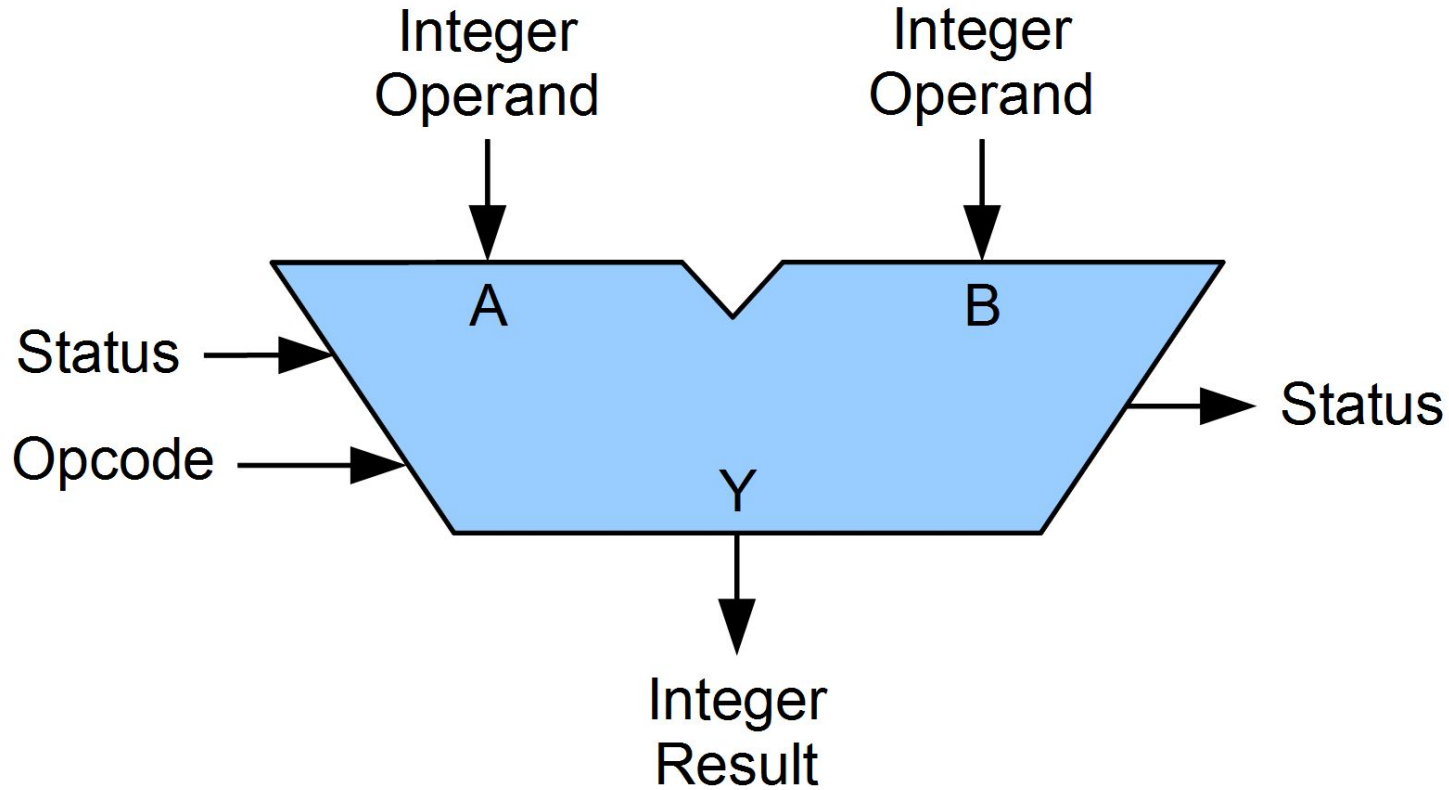

ALU Internal logic

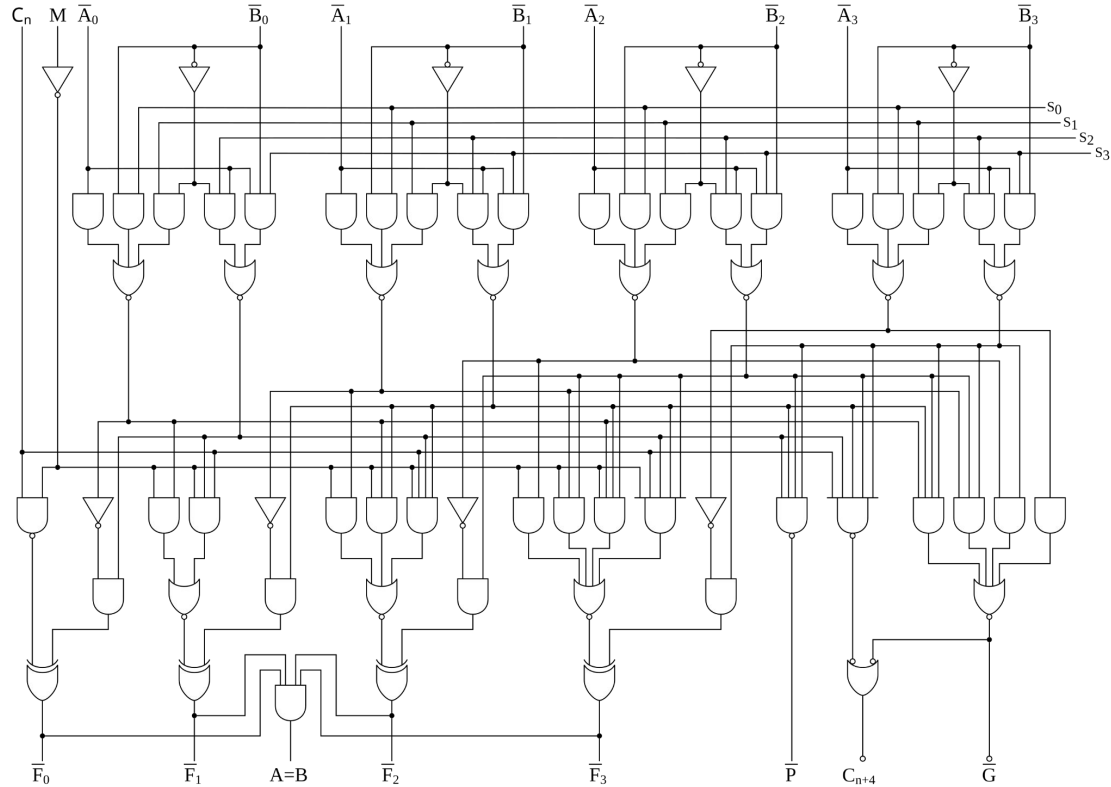

Status Registers

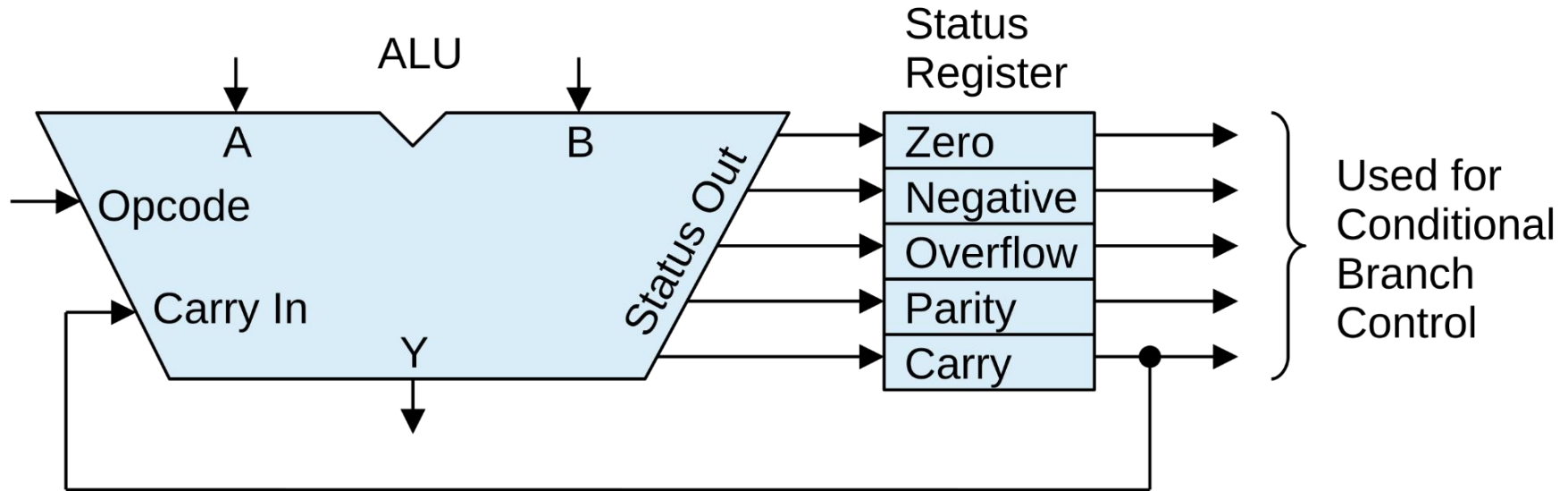

Arduino

- Uno uses ATmega328P 8 bit microcontroller
- <https://store-usa.arduino.cc/products/arduino-uno-rev3>
- <https://ww1.microchip.com/downloads/aemDocuments/documents/MCU08/ProductDocuments/DataSheets/ATmega48A-PA-88A-PA-168A-PA-328-P-DS-DS40002061B.pdf>
- <https://ww1.microchip.com/downloads/aemDocuments/documents/MCU08/ProductDocuments/ReferenceManuals/AVR-InstructionSet-Manual-DS40002198.pdf>

Instruction Cycle